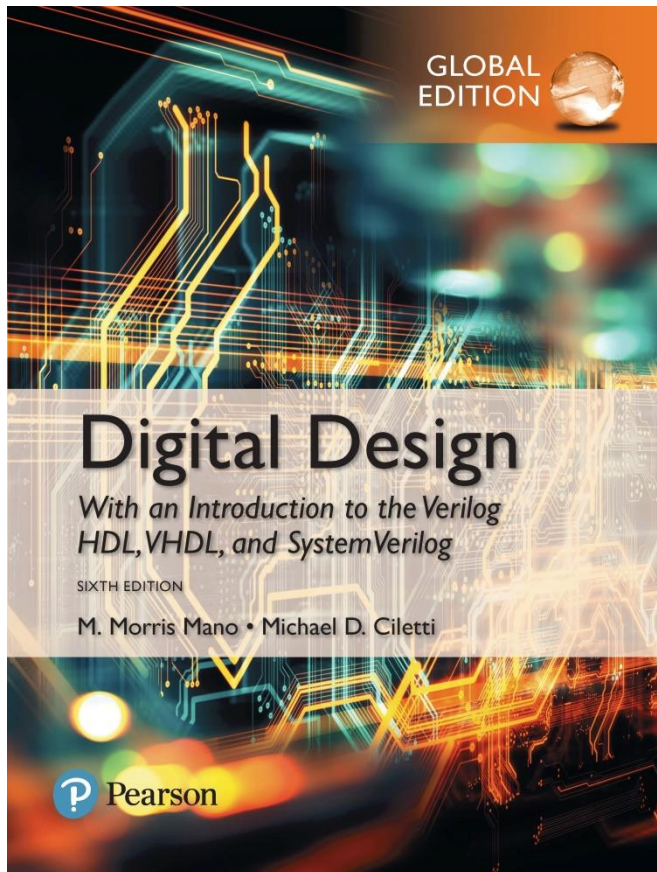


# Digital Design


With an Introduction to the Verilog HDL, VHDL, and SystemVerilog

6<sup>th</sup> Edition, Global Edition



## Chapter 04 Combinational Logic
 
## Block diagram of combinational circuit




Outputs are determined by the present inputs only

## Analysis Procedure

- To determine the function of logic
- Analysis procedure
  - Make sure the logic is combinational or sequential
  - Obtain the output Boolean functions or the truth table
- Boolean function
  - Label all gate outputs
  - Make output functions at each level
  - Substitute final outputs to input variables
- Truth table
  - Put the input variables to binary numbers
  - Determine the output value at each gate
  - Obtain truth table

## Logic diagram for analysis example

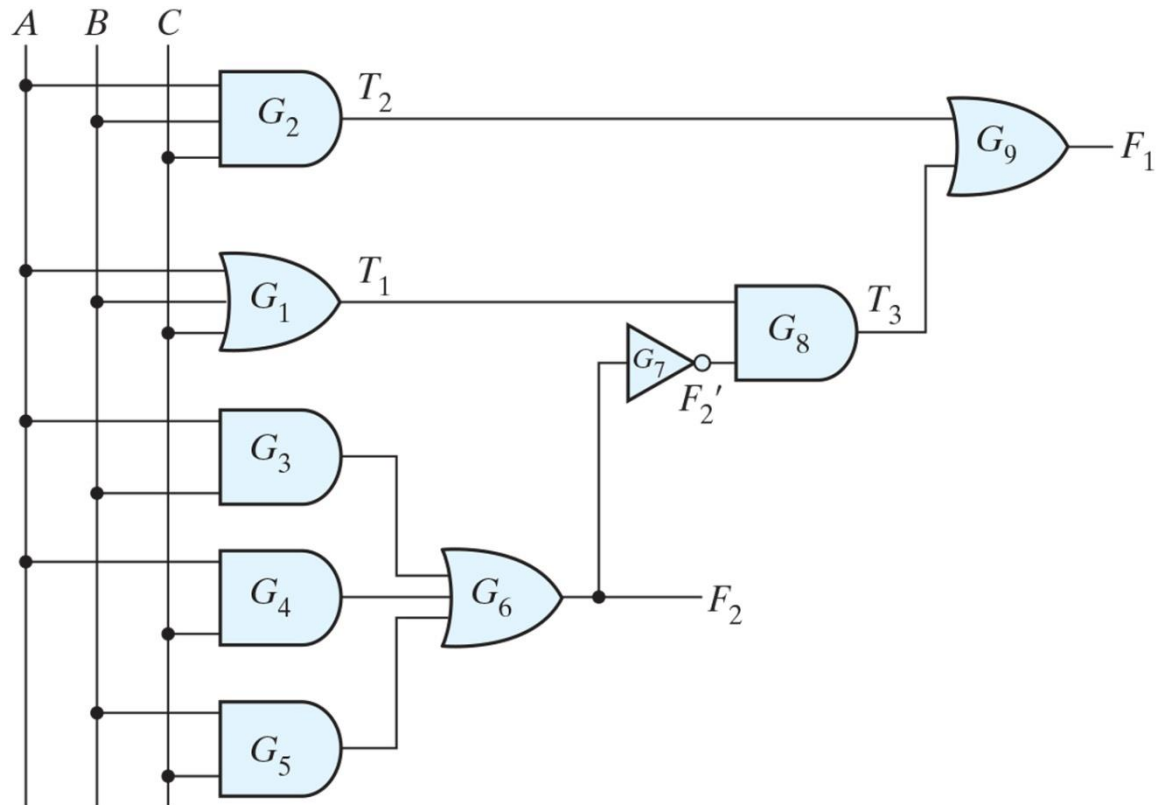

$F_1 = ?$

## Truth Table for the Logic Diagram of Fig. 4.2 (Previous slide)

<b><i>A</i></b>	<b><i>B</i></b>	<b><i>C</i></b>	<b><i>F</i><sub>2</sub></b>	<b><i>F</i>'<sub>2</sub></b>	<b><i>T</i><sub>1</sub></b>	<b><i>T</i><sub>2</sub></b>	<b><i>T</i><sub>3</sub></b>	<b><i>F</i><sub>1</sub></b>
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

## Design Procedure

- Procedure to design
  - Determine the required number of input and output from specification
  - Assign a letter symbol to each input/output
  - Derive the truth table
  - Obtain the simplified Boolean functions
  - Draw the logic diagram and verify design correctness

## Truth Table for Code Conversion Example

Input BCD				Output Excess-3 Code			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

# Maps for BCD-to-excess-3 code converter

		C			
		00	01	11	10
A	00	$m_0$ 1	$m_1$	$m_3$	$m_2$ 1
	01	$m_4$ 1	$m_5$	$m_7$	$m_6$ 1
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$ 1	$m_9$	$m_{11}$ X	$m_{10}$ X
		D			

$z = D'$

		C			
		00	01	11	10
A	00	$m_0$ 1	$m_1$	$m_3$ 1	$m_2$
	01	$m_4$ 1	$m_5$	$m_7$ 1	$m_6$
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$ 1	$m_9$	$m_{11}$ X	$m_{10}$ X
		D			

$y = CD + C'D'$

		C			
		00	01	11	10
A	00	$m_0$	$m_1$ 1	$m_3$ 1	$m_2$ 1
	01	$m_4$ 1	$m_5$	$m_7$	$m_6$
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$	$m_9$ 1	$m_{11}$ X	$m_{10}$ X
		D			


$x = B'C + B'D + BC'D'$

		C			
		00	01	11	10
A	00	$m_0$	$m_1$	$m_3$	$m_2$
	01	$m_4$	$m_5$ 1	$m_7$ 1	$m_6$ 1
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$ 1	$m_9$ 1	$m_{11}$ X	$m_{10}$ X
		D			

$w = A + BC + BD$


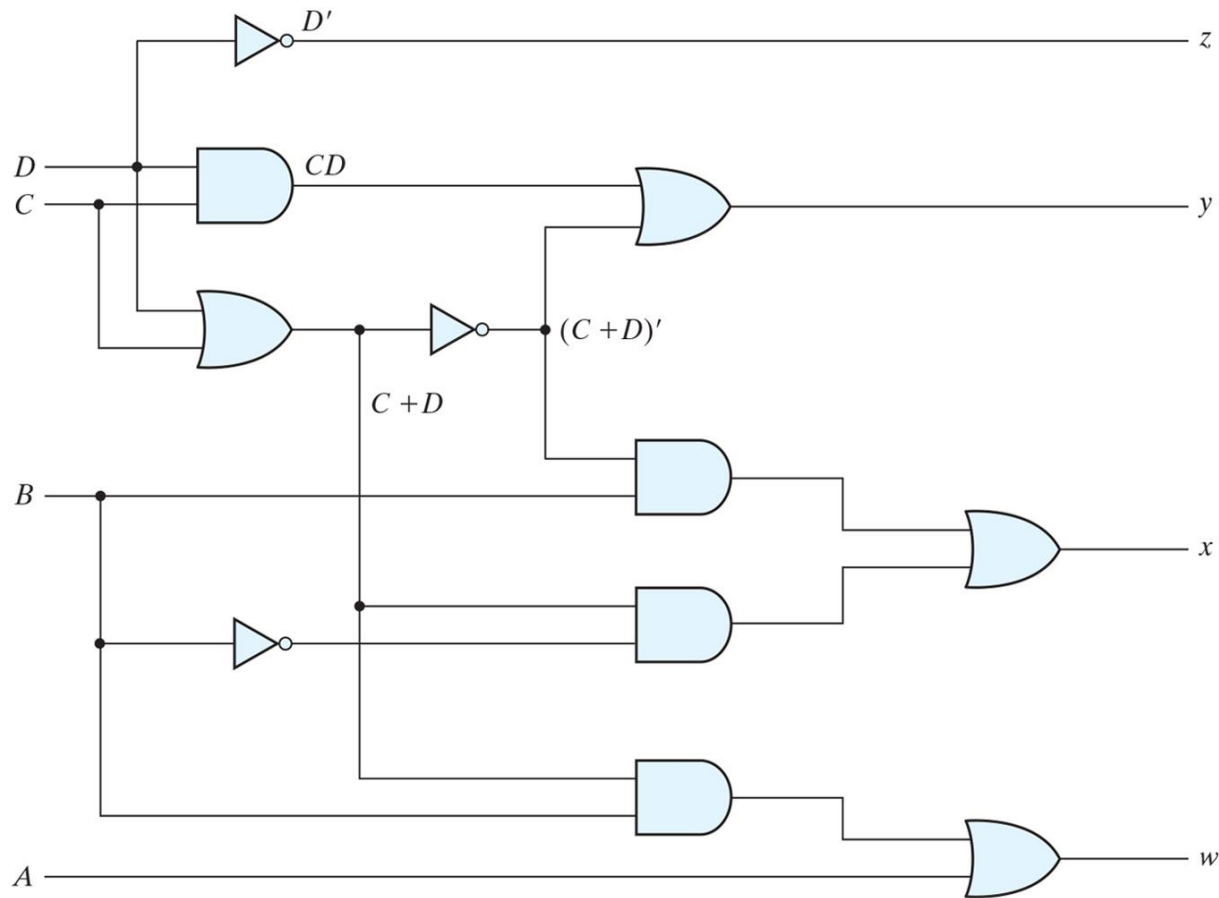
## Logic diagram for BCD-to-excess-3 code converter



## Half Adder



<b><i>x</i></b>	<b><i>y</i></b>	<b><i>c</i></b>	<b><i>s</i></b>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- Sum of 2 binary inputs
- Input : X(augend), Y(addend)
- Output : S(sum), C(carry)

$$S = xy' + x'y$$

$$C = xy$$

## Implementation of half adder

  

## Full Adder

<i>x</i>	<i>y</i>	<i>z</i>	<i>C</i>	<i>S</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- Sum of 3 binary inputs
- Input : X,Y(2 significant bits),Z(1 carry bit)
- Output : S(sum),C(carry)

## K-Maps for full adder


		$y$			
		$yz$		00	01
$x$	0	$m_0$	$m_1$ 1	$m_3$	$m_2$ 1
	1	$m_4$ 1	$m_5$	$m_7$ 1	$m_6$

(a)  $S = x'y'z + x'yz' + xy'z' + xyz$


		$y$			
		$yz$		00	01
$x$	0	$m_0$	$m_1$	$m_3$ 1	$m_2$
	1	$m_4$	$m_5$ 1	$m_7$ 1	$m_6$ 1

(b)  $C = xy + xz + yz$

 
## Implementation of full adder in sum-of-products form


 
## Implementation of full adder with two half adders and an OR gate




## Four-bit adder

 

Subscript $i$ :	3	2	1	0	
Input carry	0	1	1	0	$C_i$
Augend	1	0	1	1	$A_i$
Addend	0	0	1	1	$B_i$
Sum	1	1	1	0	$S_i$
Output carry	0	0	1	1	$C_{i+1}$




## Full adder with $P$ and $G$ shown

 


- Delay time increase (carry delay)
- One solution is **carry lookahead**
- All carry is a function of  $P_i, G_i$  and  $C_0$
 
## Logic diagram of carry lookahead generator



## Four-bit adder with carry lookahead

 

$C_0$  = input carry

$$C_1 = G_0 + P_0C_0$$

$$C_2 = G_1 + P_1C_1 = G_1 + P_1(G_0 + P_0C_0) = G_1 + P_1G_0 + P_1P_0C_0$$

$$C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$$


## Overflow

- Sum of  $n$  digit number occupies  $n+1$  digit
- Occurs when two numbers are same sign
- (examples of overflow)

carries:	0	1	
+70	0	1000110	
+80	0	1010000	
<hr/>			
+150	1	0010110	

carries:	1	0	
-70	1	0111010	
-80	1	0110000	
<hr/>			
-150	0	1101010	

 
## Four-bit adder-subtractor (with overflow detection)



## Derivation of BCD Adder

Binary Sum					BCD Sum					Decimal
<i>K</i>	<i>Z</i> <sub>8</sub>	<i>Z</i> <sub>4</sub>	<i>Z</i> <sub>2</sub>	<i>Z</i> <sub>1</sub>	<i>C</i>	<i>S</i> <sub>8</sub>	<i>S</i> <sub>4</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>1</sub>	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

# Block diagram of a BCD adder

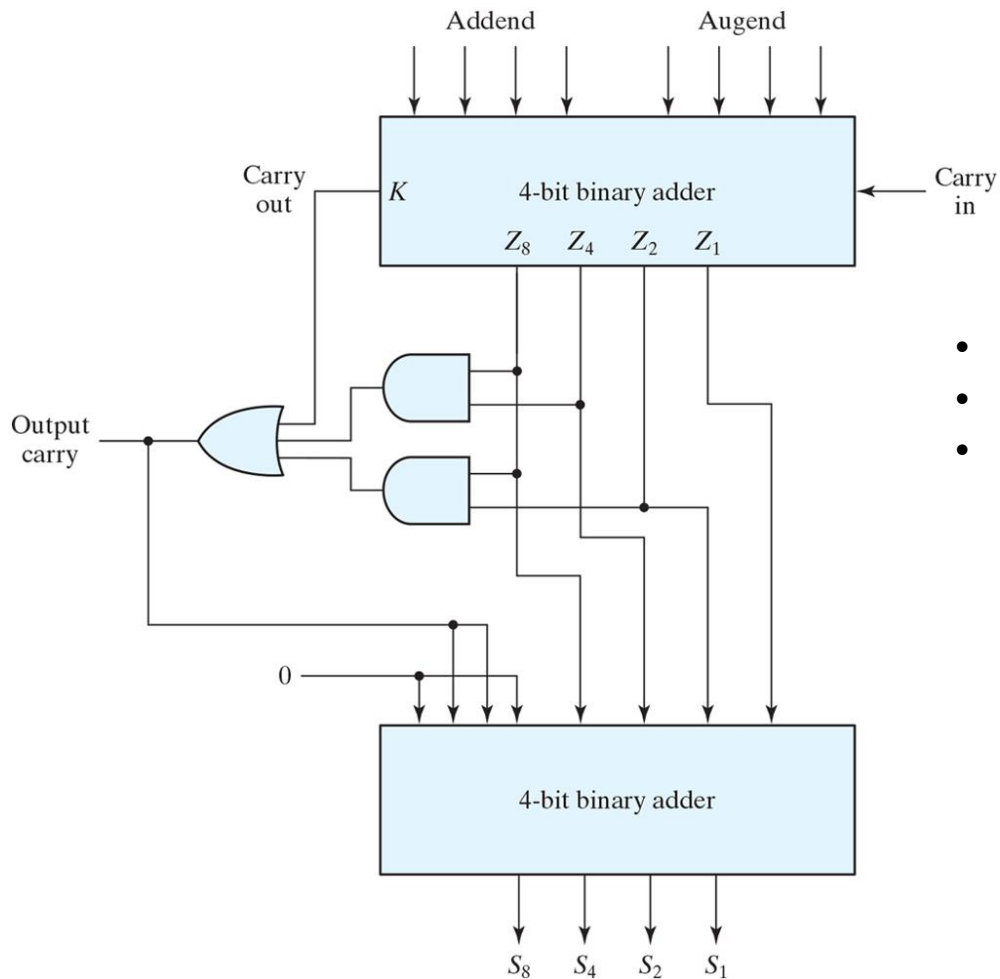


- BCD digit output of 2-BCD digit sum
- Carry occurs if output 1010~1111
- $C = K + Z_8 Z_4 + Z_8 Z_2$

1100	1010
1101	1011
1110	
1111	

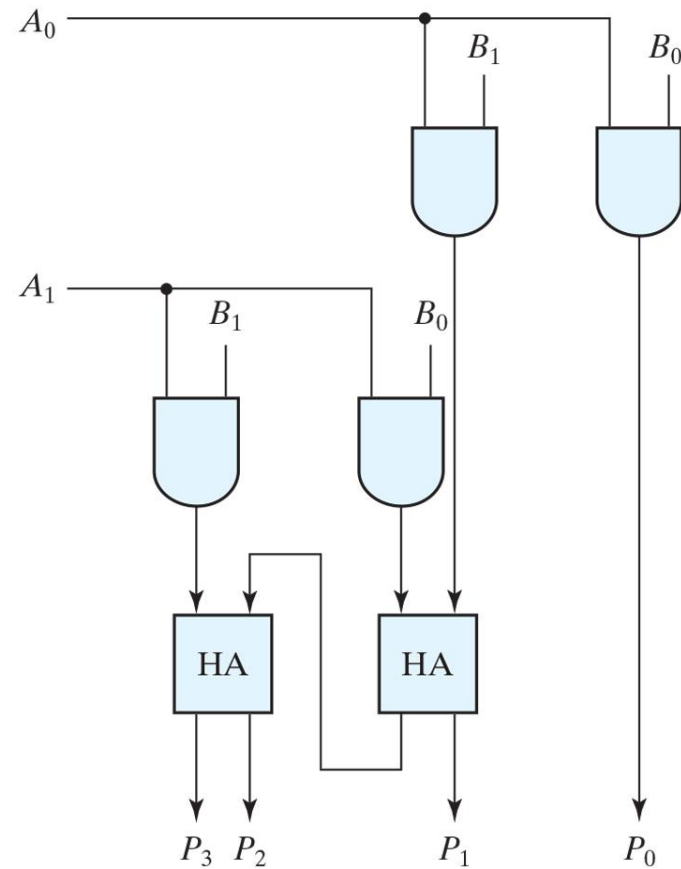
## Two-bit by two-bit binary multiplier

$$\begin{array}{r} \phantom{A_1} B_1 \phantom{A_0} B_0 \\ A_1 \phantom{A_0} \\ \hline A_0 B_1 \phantom{A_0} A_0 B_0 \\ \phantom{A_1} A_1 B_1 \phantom{A_0} A_1 B_0 \\ \hline P_3 \phantom{P_2} P_2 \phantom{P_1} P_1 \phantom{P_0} \end{array}$$





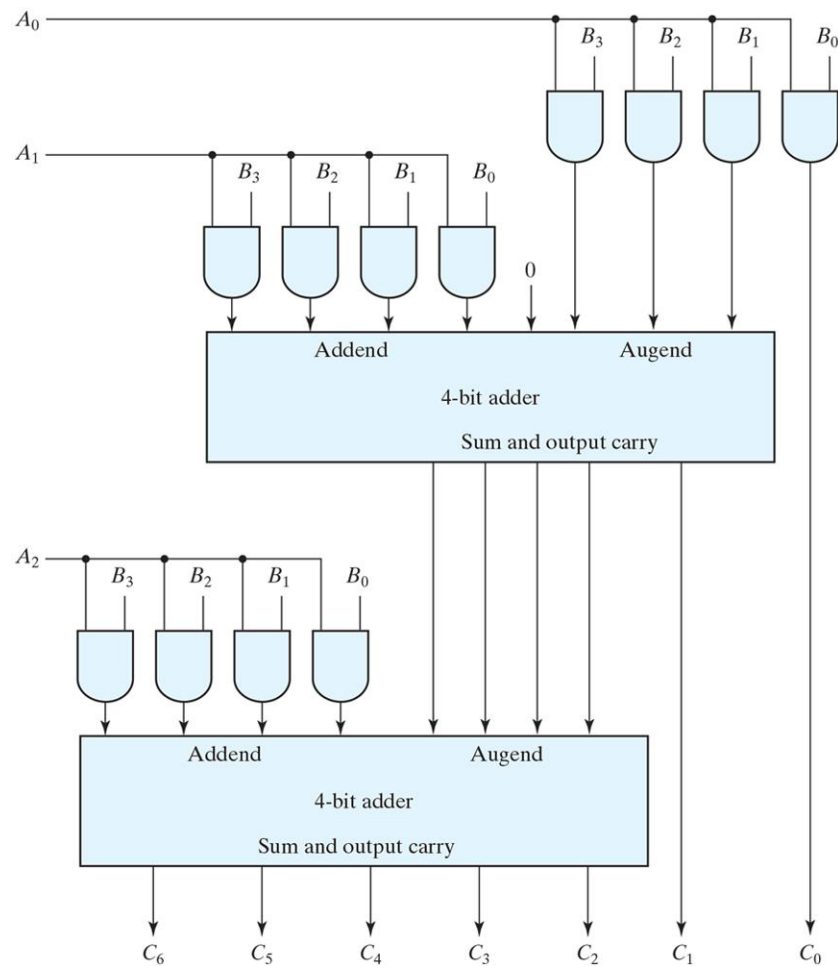
# Four-bit by three-bit binary multiplier



## Four-bit magnitude comparator

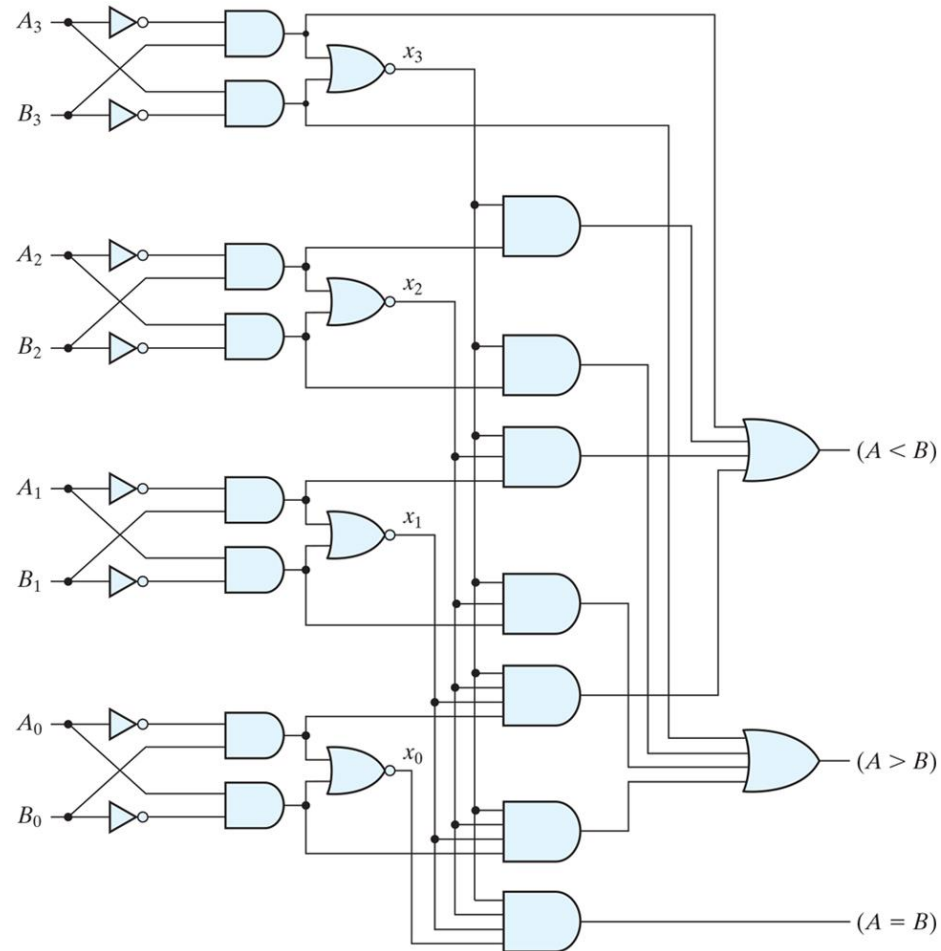


## Decoder


- Generate the  $2^n$ (or less) minterms of  $n$  input variables
  - Eg) 3 to 8 line decoder

Inputs			Outputs							
<i>x</i>	<i>y</i>	<i>z</i>	<i>D</i> <sub>0</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>3</sub>	<i>D</i> <sub>4</sub>	<i>D</i> <sub>5</sub>	<i>D</i> <sub>6</sub>	<i>D</i> <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

## Three-to-eight-line decoder

 
 
## Two-to-four-line decoder with enable input



$E$	$A$	$B$	$D_0$	$D_1$	$D_2$	$D_3$
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

## 4 x 16 decoder constructed with two 3 x 8 decoders


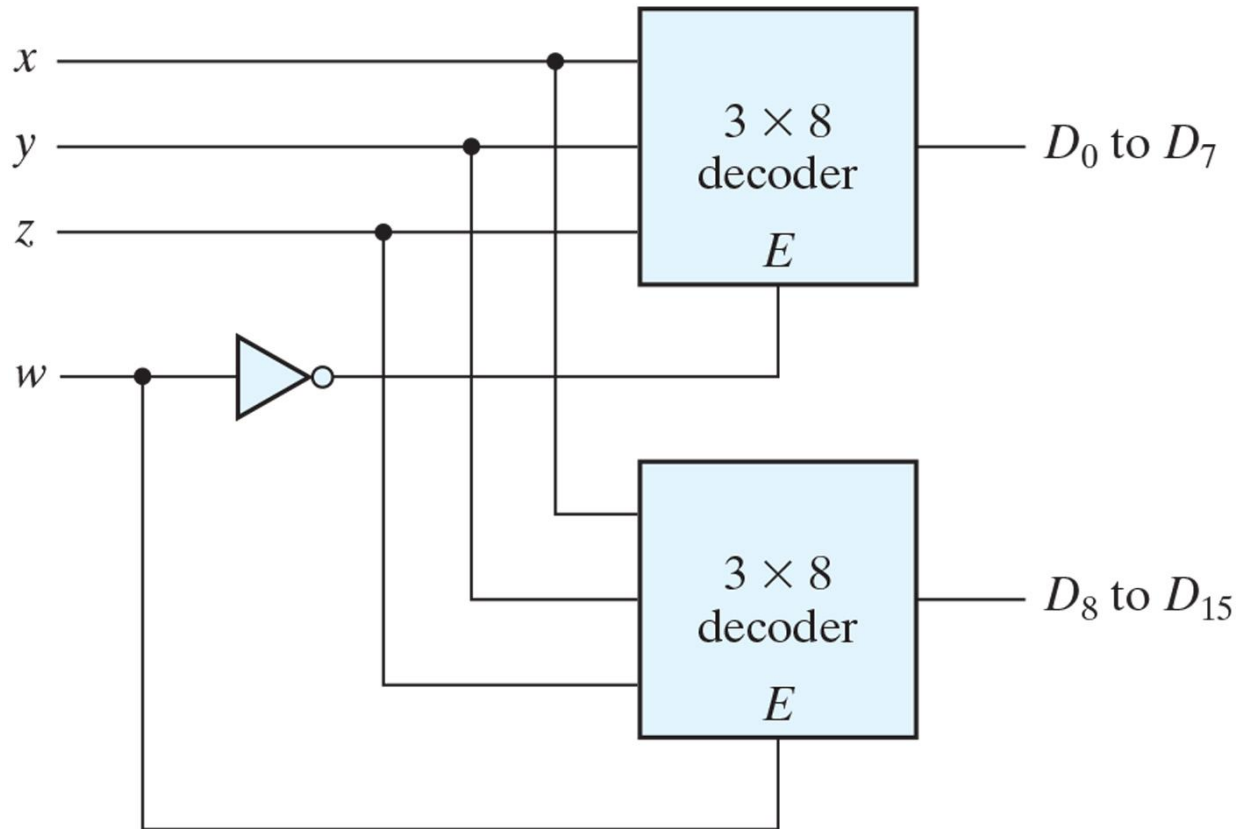



Figure PE4.8

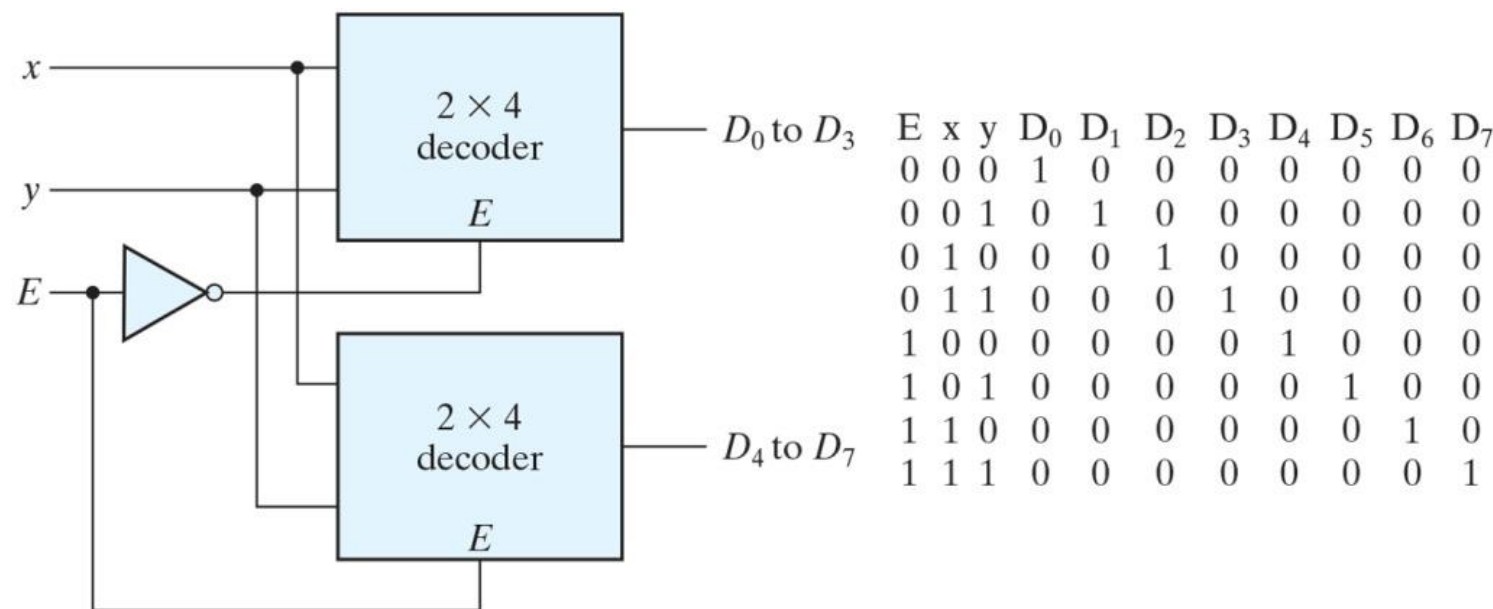

# Implementation of a full adder with a decoder

**Table 4-4**  
*Full Adder*

$x$	$y$	$z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

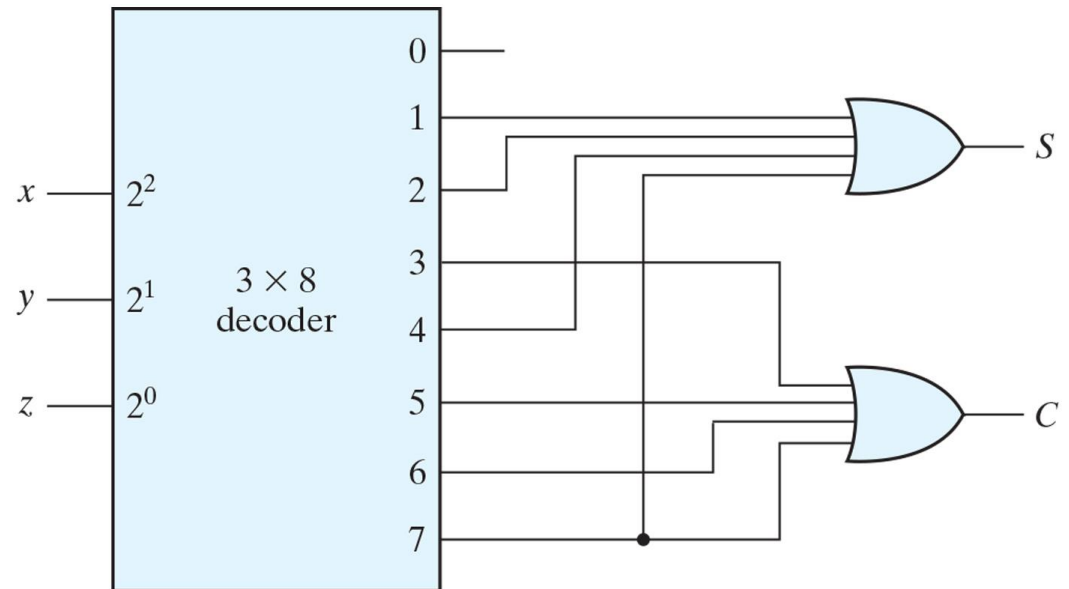





## Encoder

- Inverse operation of a decoder
- Generate  $n$  outputs of  $2^n$  input values
  - Eg) octal to binary encoder


Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$x$	$y$	$z$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

# Truth Table of a Priority Encoder

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

  


# Four-input priority encoder

 

 
## Multiplexer (MUX)

- Select a binary information from many input lines
- Selection is controlled by a set of selection lines
- $2^n$  input lines have  $n$  selection lines




(a) Logic diagram

 

(b) Block diagram

# Four-to-one-line multiplexer

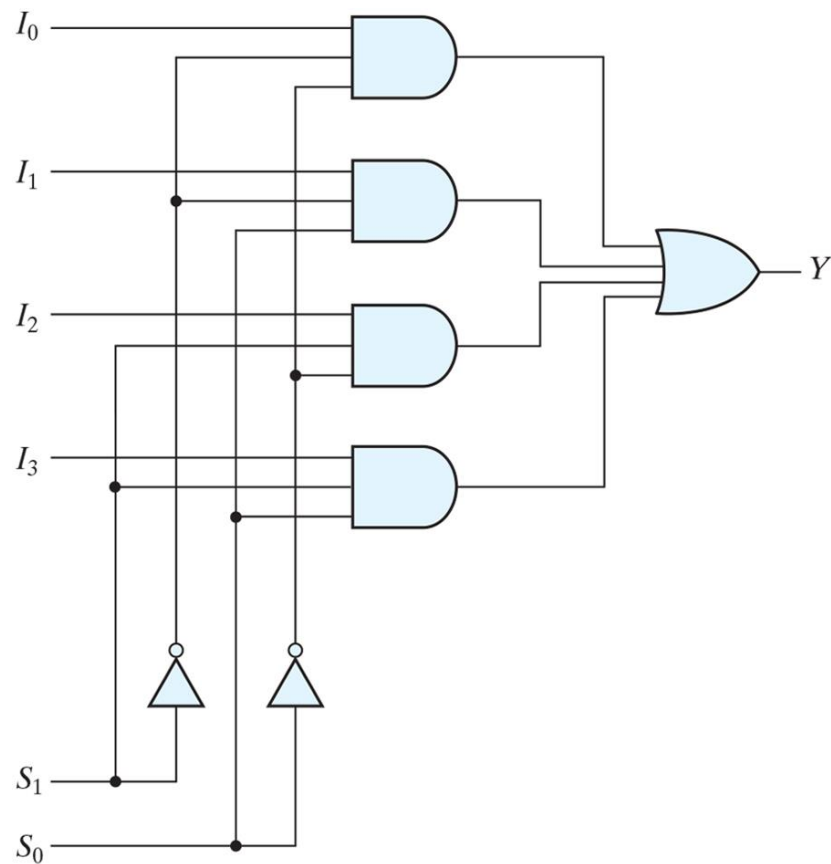


(a) Logic diagram

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

(b) Function table

# Quadruple two-to-one-line multiplexer

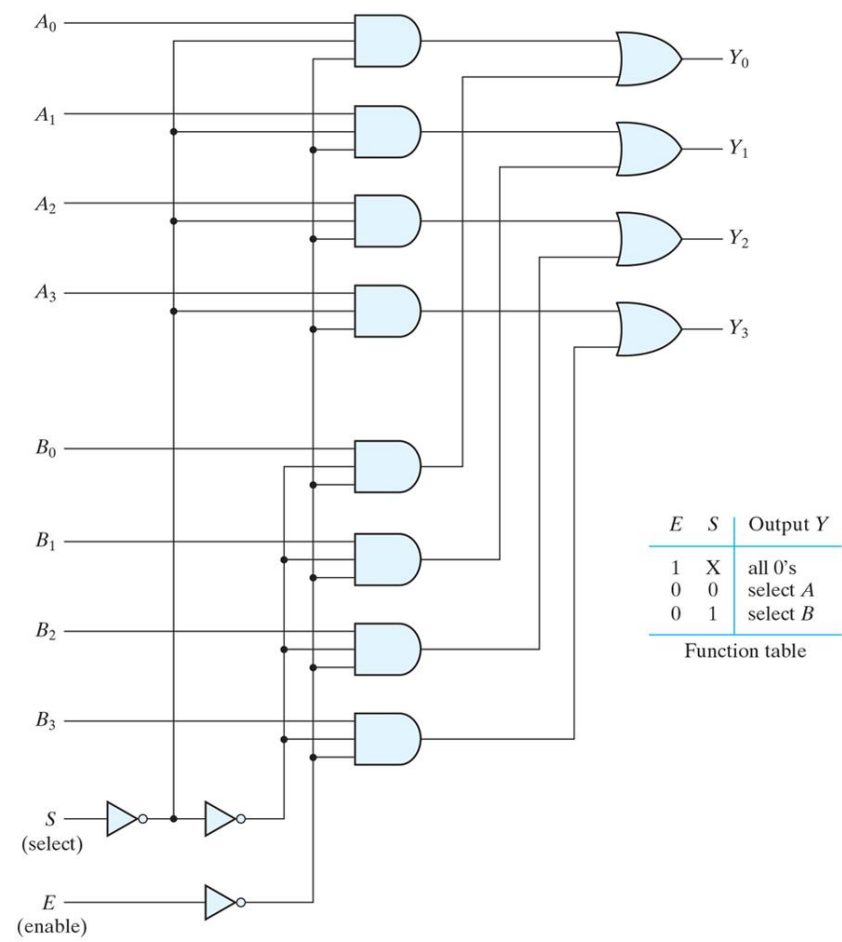


## Implementing a Boolean function with a multiplexer

- Minterms of function are generated in a MUX
- $n$  input variables,  $n-1$  selection input

$x$	$y$	$z$	$F$	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	


(a) Truth table

 

(b) Multiplexer implementation


# Implementing a four-input function with a multiplexer

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

 



 
## Graphic symbol for a three-state buffer




*High-impedance* behaves like an open circuit

# Multiplexers with three-state gates

 

(a) 2-to-1-line mux

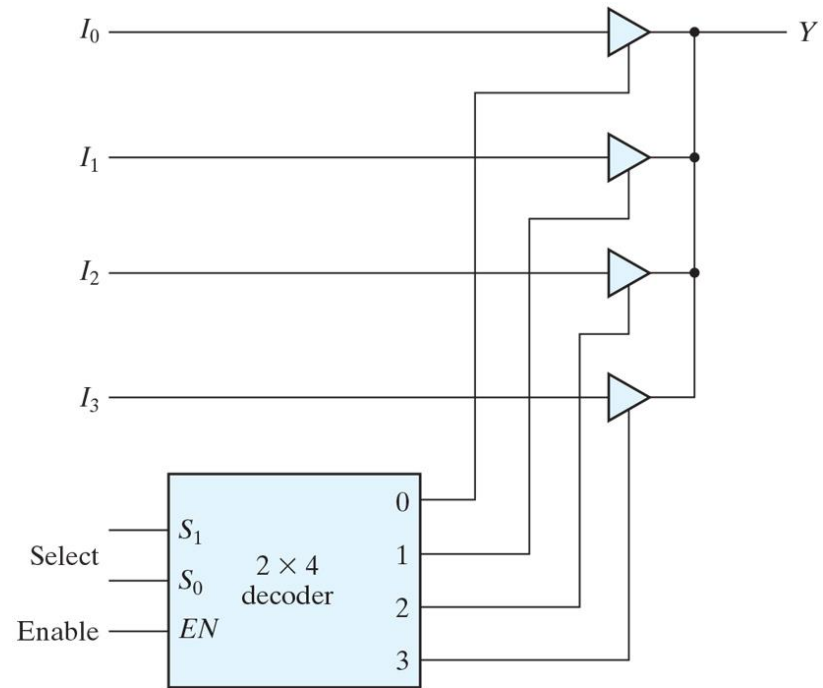

(b) 4-to-1-line mux