 


Digital Design

With an Introduction to the Verilog HDL, VHDL, and SystemVerilog

6th Edition, Global Edition



Chapter 07

Memory and Programmable Logic


Introduction

Memory


- **RAM**(random access memory): read and write operation
- **ROM**(read only memory) : only read operation

Volatile?

 Conventional and array logic diagrams for OR gate.




(a) Conventional symbol

 

(b) Array logic symbol

Block diagram of a memory unit.

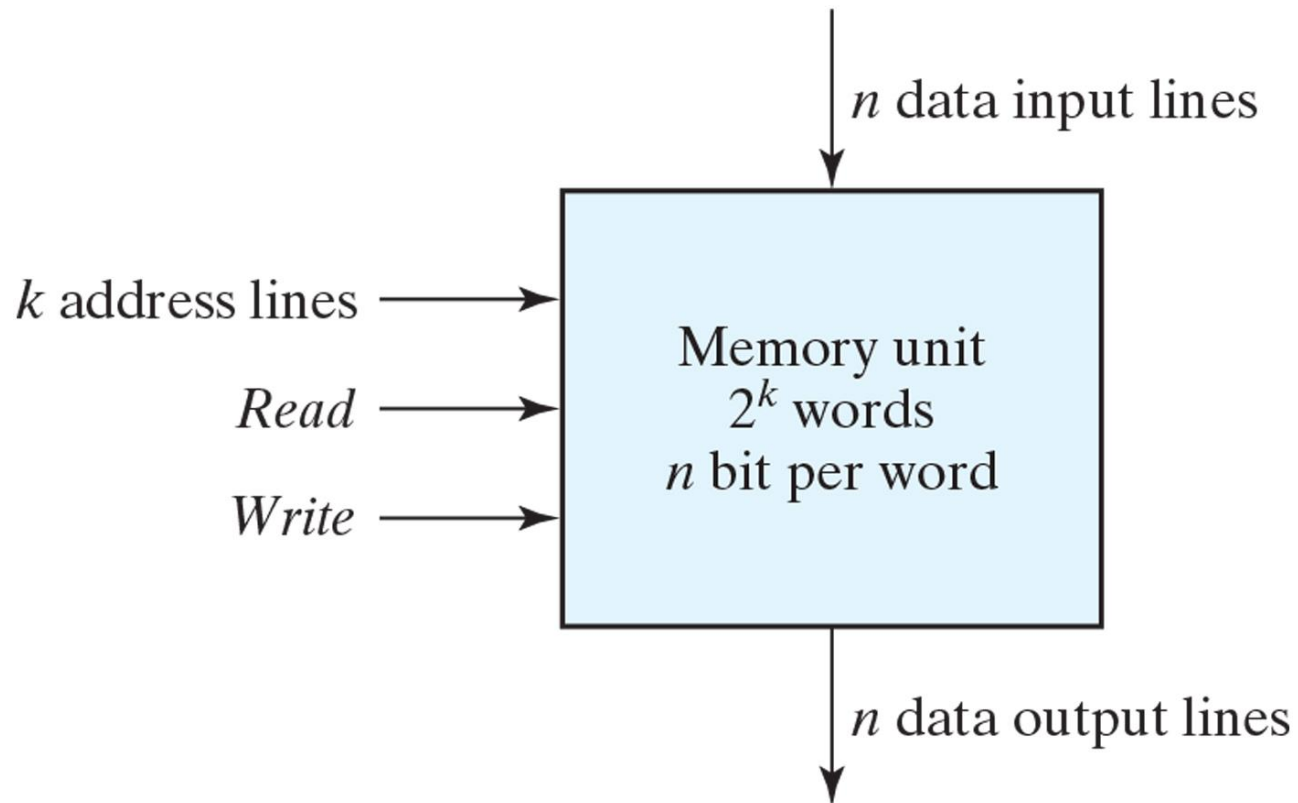



Contents of a 1024 × 16 memory.

Memory address		Memory content
Binary	Decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101


Control Inputs to Memory Chip.

Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word


Memory cycle timing waveforms.

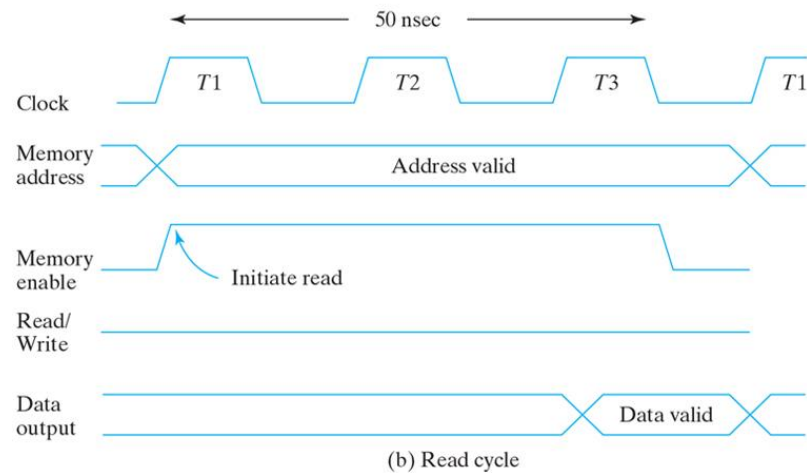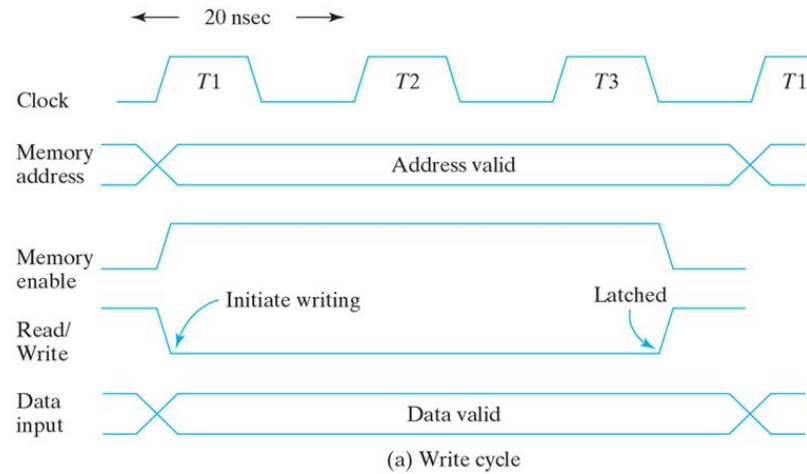

Memory cell.

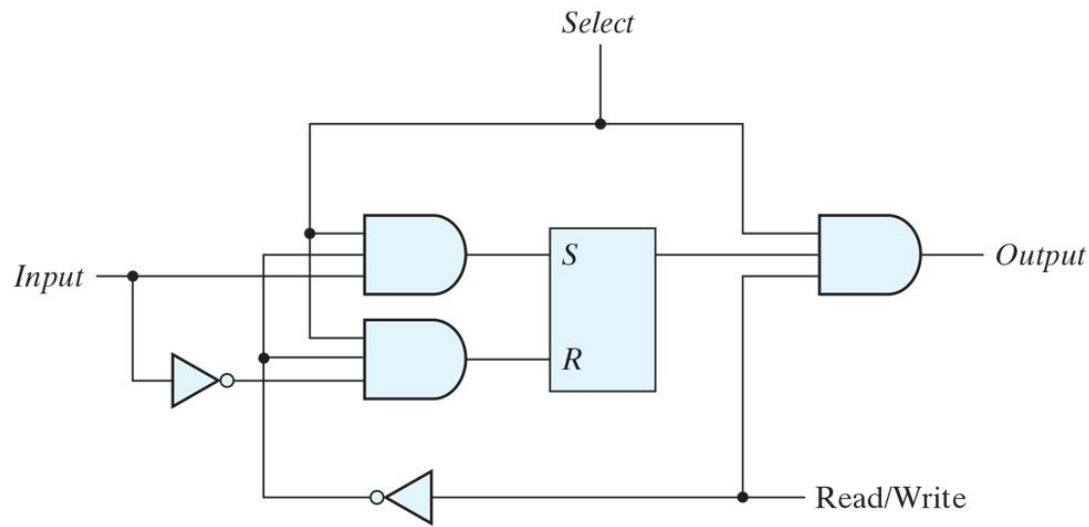


(a) Logic diagram

 


(b) Block diagram


Diagram of a 4×4 RAM.

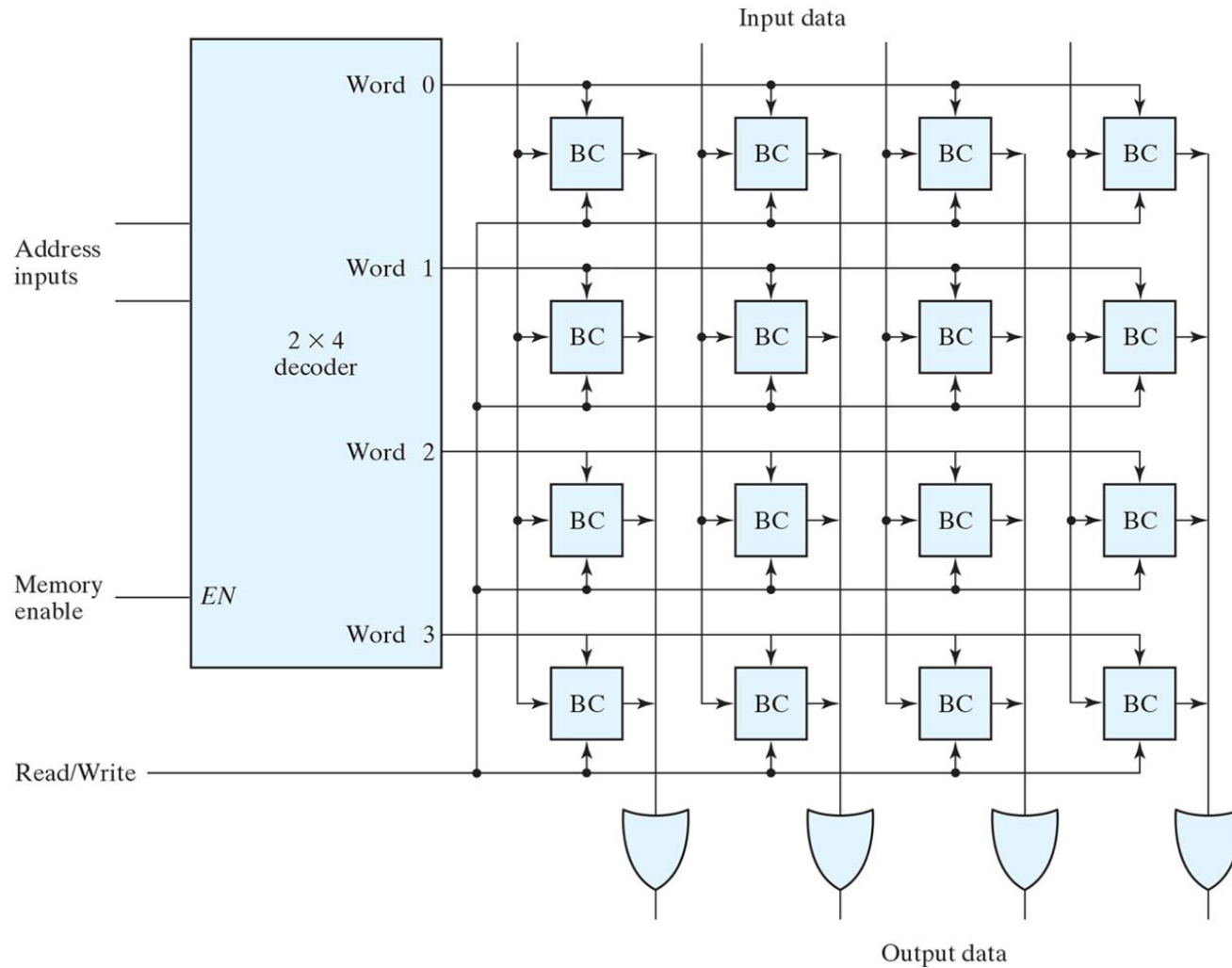

 
Two-dimensional decoding structure for a 1K-word memory.




Address multiplexing for a 64K DRAM.

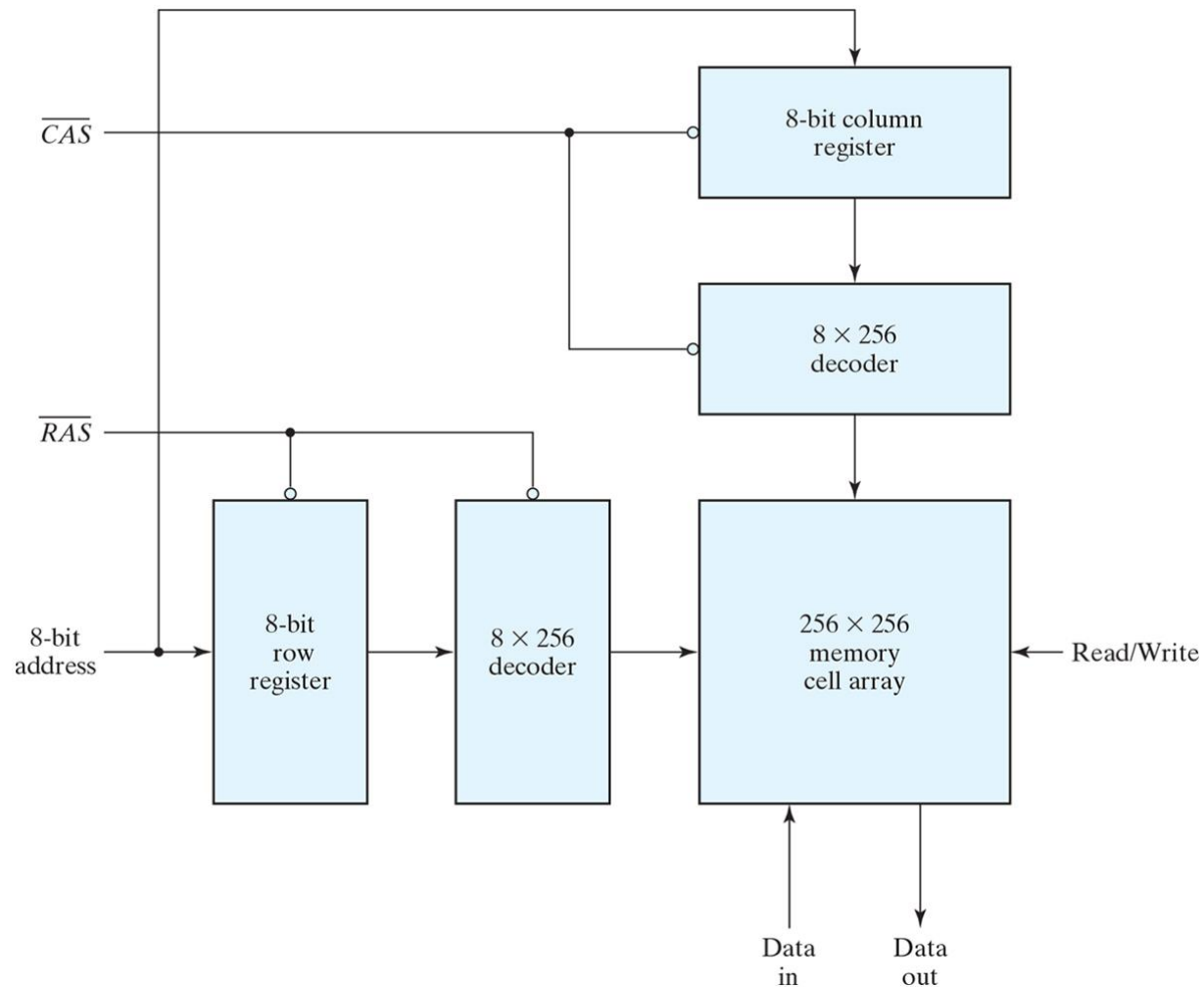

ROM block diagram.

 


Internal logic of a 32×8 ROM.

 


ROM Truth Table (Partial).

Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		\vdots							\vdots			
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

 Programming the ROM according to the previous Table



Basic configuration of three PLDs.

 

(a) Programmable read-only memory (PROM)



(b) Programmable array logic (PAL)



(c) Programmable logic array (PLA)

PLA Programming

$$F_1(A, B, C) = \sum (0, 1, 2, 4)$$

$$F_2(A, B, C) = \sum (0, 5, 6, 7)$$

$$F_1 = (AB + AC + BC)'$$

$$F_2 = AB + AC + A'B'C'$$

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	1	0	1
<i>A</i>	1	1	0	0	0

$\underbrace{\hspace{10em}}_C$

$$F_1 = A'B' + A'C' + B'C'$$

$$F_1 = (AB + AC + BC)'$$

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	0	0	0
<i>A</i>	1	0	1	1	1

$\underbrace{\hspace{10em}}_C$


$$F_2 = AB + AC + A'B'C'$$

$$F_2 = (A'C + A'B + AB'C')'$$


PLA programming table						
	Product term	Inputs			Outputs	
		<i>A</i>	<i>B</i>	<i>C</i>	(C) <i>F</i> ₁	(T) <i>F</i> ₂
<i>AB</i>	1	1	1	–	1	1
<i>AC</i>	2	1	–	1	1	1
<i>BC</i>	3	–	1	1	1	–
<i>A'B'C'</i>	4	0	0	0	–	1

Fig. 7-15 Solution to Example 7-2

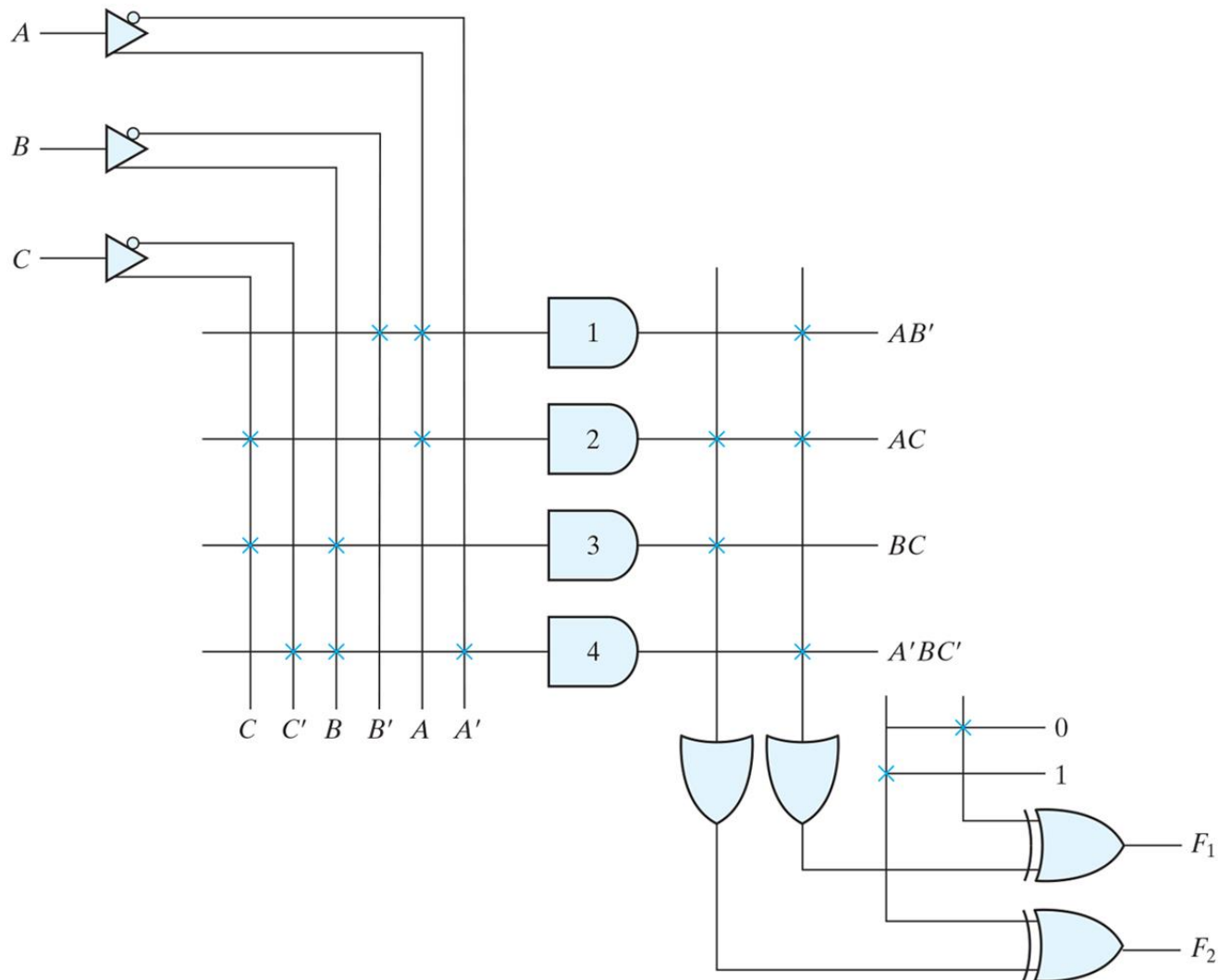PLA with three inputs, four product terms, and two outputs.



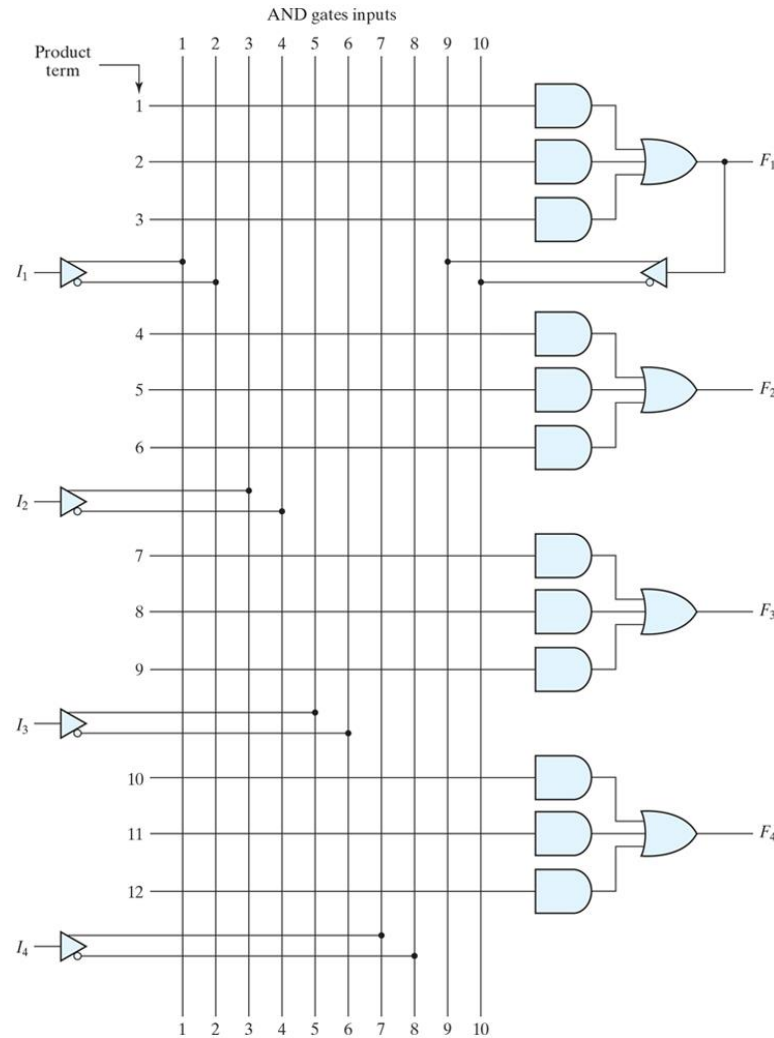PAL with four inputs, four outputs, and a three-wide AND–OR structure.



PAL Programming Table.

$$w(A, B, C, D) = \sum(2, 12, 13)$$

$$x(A, B, C, D) = \sum(7, 8, 9, 10, 11, 12, 14, 15)$$

$$y(A, B, C, D) = \sum(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A, B, C, D) = \sum(1, 2, 8, 12, 13,)$$

$$w = ABC' + A'B'CD'$$

$$x = A + BCD$$


$$y = A'B + CD + B'D'$$

$$z = ABC' + A'B'CD' + AC'D' + A'B'C'D$$


$$= w + AC'D' + A'B'C'D$$

Product Term	AND Inputs				w	Outputs
	A	B	C	D		
1	1	1	0	—	—	$w = ABC' + A'B'CD'$
2	0	0	1	0	—	
3	—	—	—	—	—	
4	1	—	—	—	—	$x = A + BCD$
5	—	1	1	1	—	
6	—	—	—	—	—	
7	0	1	—	—	—	$y = A'B + CD + B'D'$
8	—	—	1	1	—	
9	—	0	—	0	—	
10	—	—	—	—	1	$z = w + AC'D' + A'B'C'D$
11	1	—	0	0	—	
12	0	0	0	1	—	


Fuse map for PAL

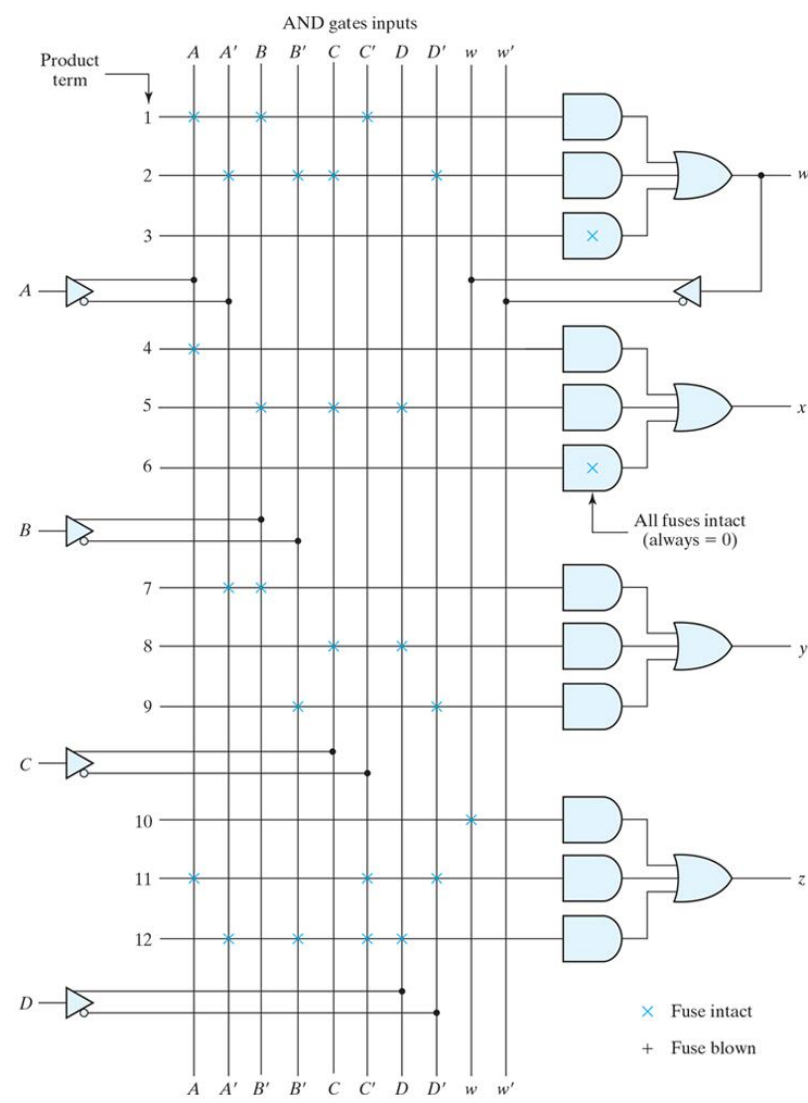


Sequential programmable logic device.

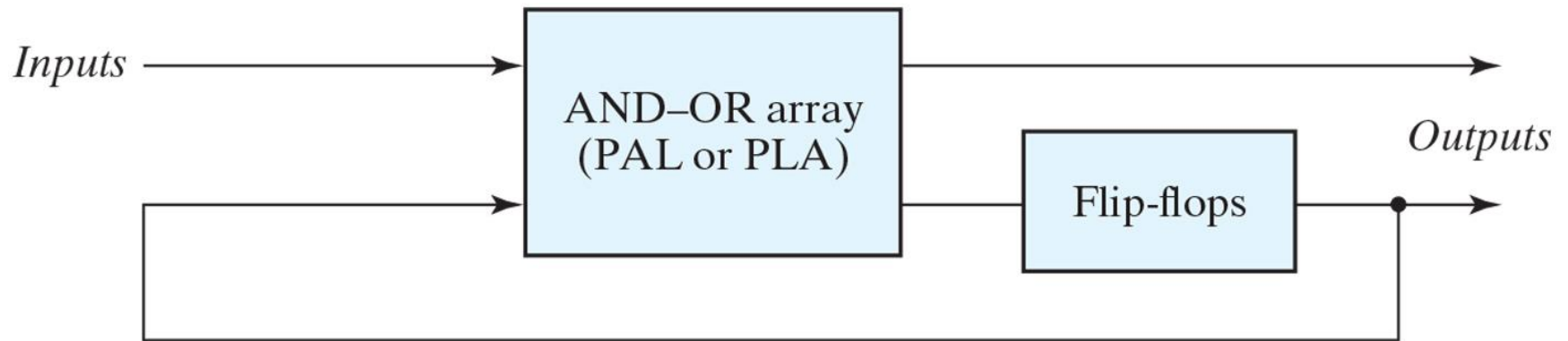


Basic macrocell logic.

 


General CPLD configuration.

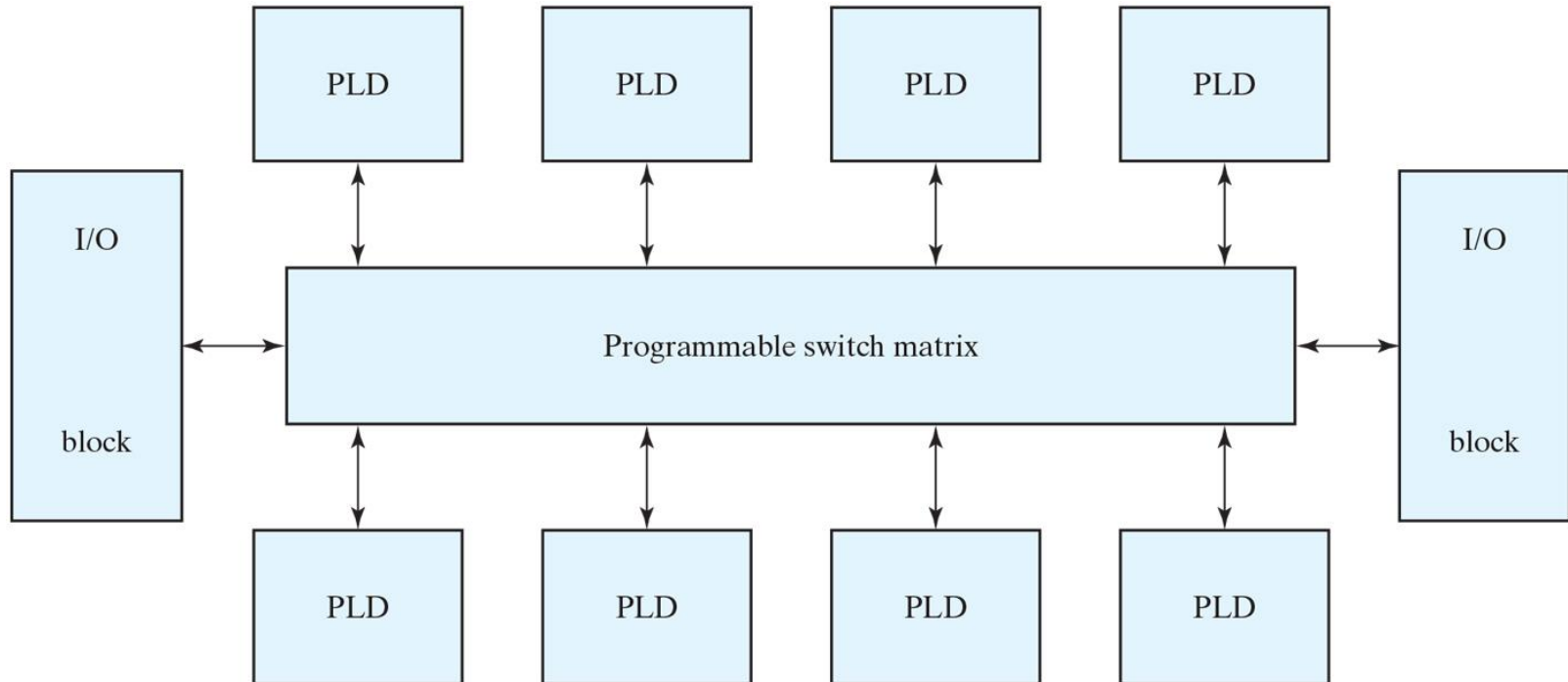

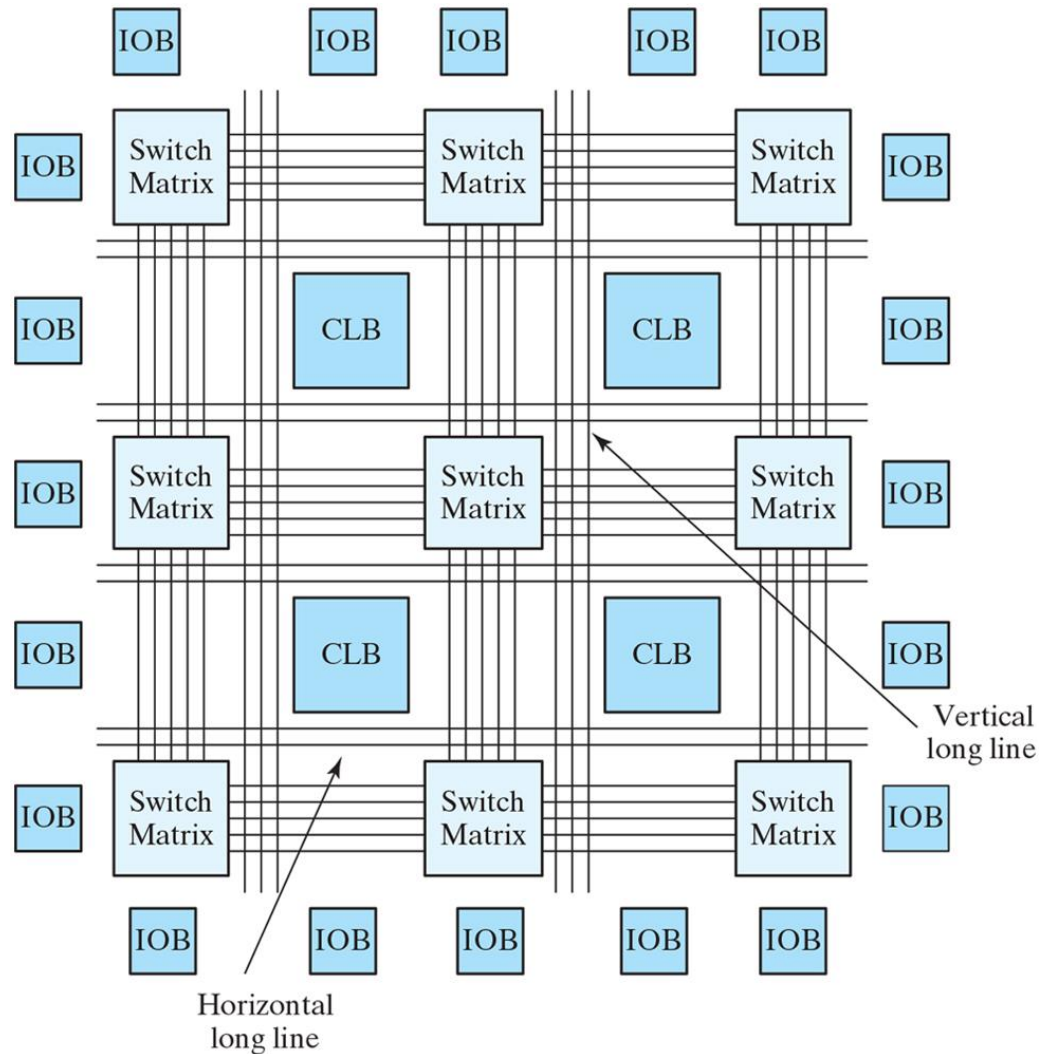Basic architecture of Xilinx Spartan and predecessor devices.



CLB architecture.

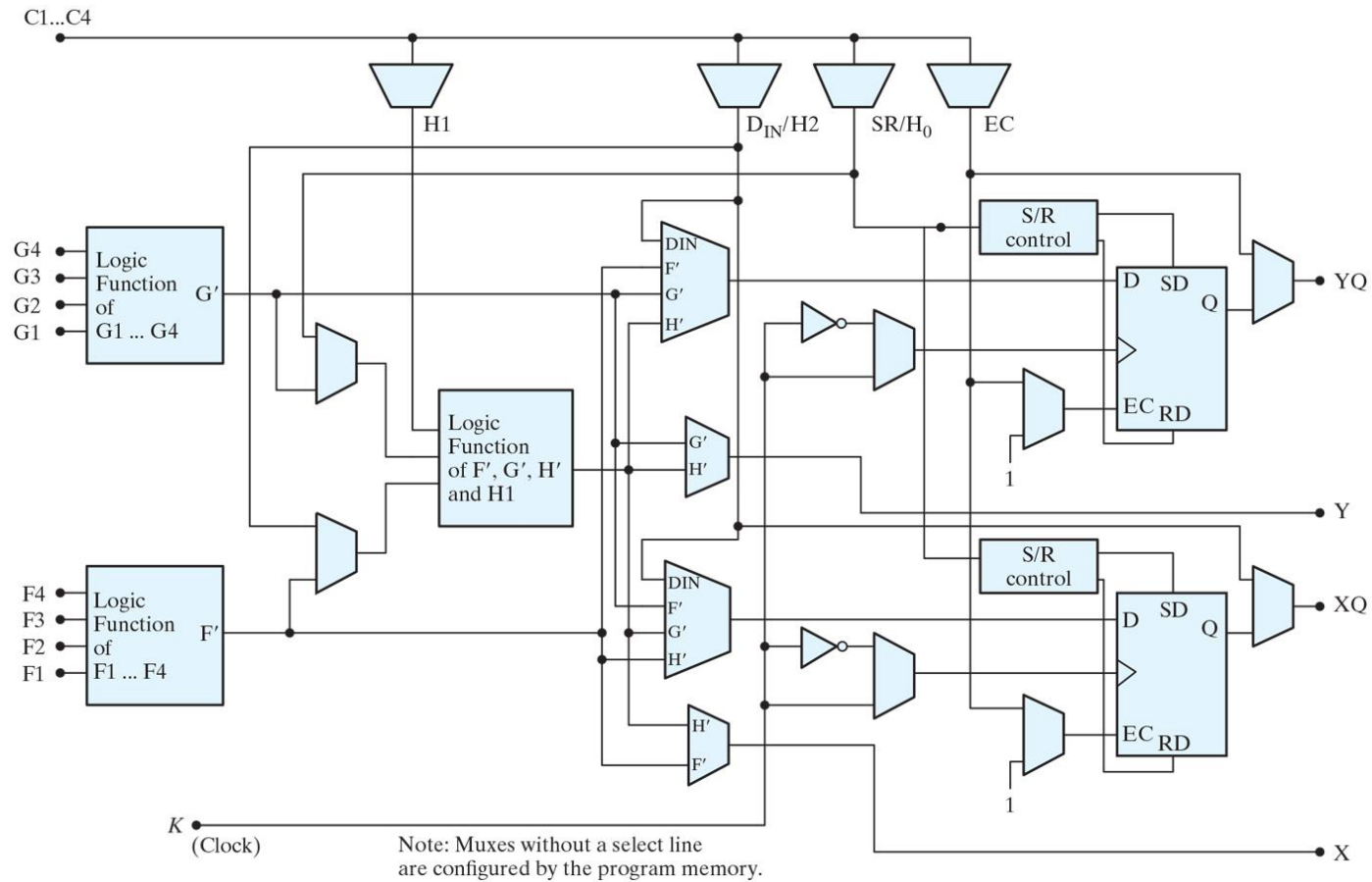

Xilinx Spartan II architecture.

