 


Digital Design

With an Introduction to the Verilog HDL, VHDL, and SystemVerilog


6th Edition, Global Edition



Chapter 05


Synchronous Sequential Logic

Block diagram of sequential circuit

 

- Outputs are function of inputs and present states
- Present states are supplied by memory elements

Synchronous clocked sequential circuit

 


(a) Block diagram



(b) Timing diagram of clock pulses

- Two types of sequential logic
 - Synchronous : behavior depends on the signals affecting storage elements at discrete time
 - Asynchronous : behavior depends on inputs at any instance of time

SR latch with NOR gates

 


(a) Logic diagram

S	R	Q	Q'
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$)
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$)
1	1	0	0 (forbidden)

(b) Function table

- $S=1, R=0$ then $Q=1$ (set)
- $S=0, R=1$ then $Q=0$ (reset)
- $S=0, R=0$ then no change (keep condition)
- $S=1, R=1$ $Q=Q'=0$ (undefined)


SR latch with NAND gates

 

S	R	Q	Q'	
1	0	0	1	
1	1	0	1	(after $S = 1, R = 0$)
0	1	1	0	
1	1	1	0	(after $S = 0, R = 1$)
0	0	1	1	(forbidden)

(b) Function table

SR latch with control input

 


(a) Logic diagram

En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table

D latch



 


(a) Logic diagram

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

(b) Function table

Graphic symbols for latches

   

Clock response in latch and flip-flop



(a) Response to positive level




(b) Positive-edge response



(c) Negative-edge response


- Latch : case (a), output changes as input changes
- Flip-flop : output only changes at clock edge

Master-slave *D* flip-flop

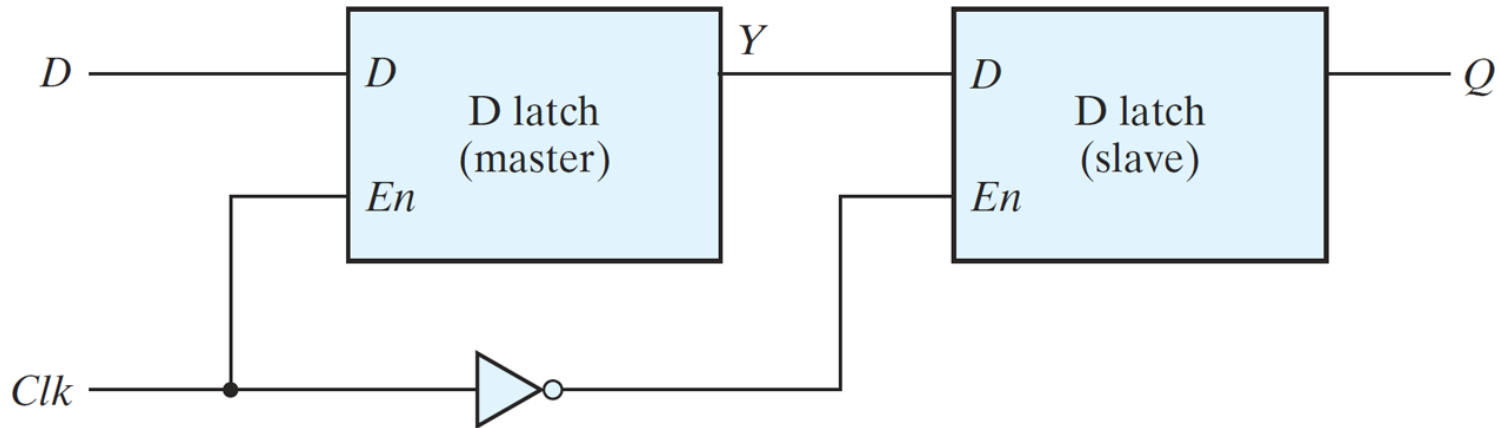


- Negative edge triggered D flip-flop
- $Clk=0$: master disable, slave enable
 - Output has no relation with input
- $Clk=1$: master enable, slave disable

 Graphic symbol for edge-triggered *D* flip-flop




(a) Positive-edge

 


(b) Negative-edge

JK flip-flop

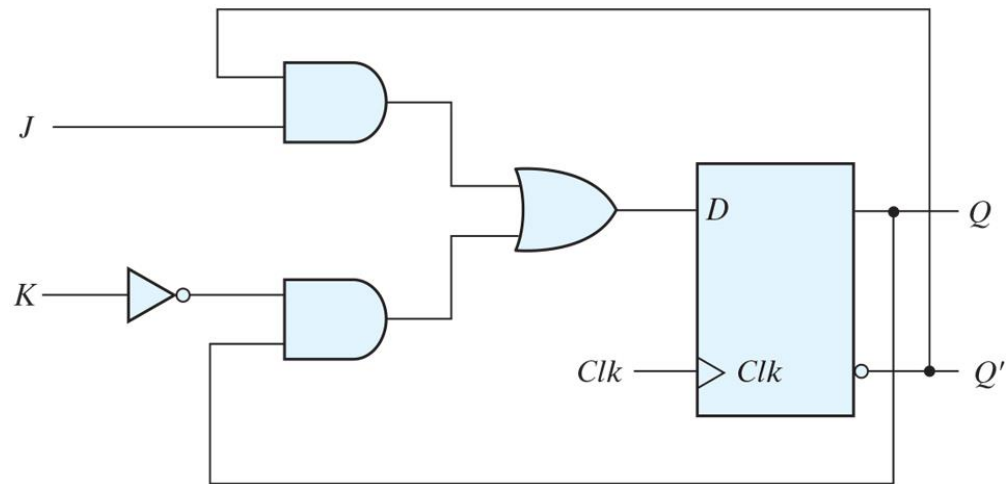


(a) Circuit diagram

 

(b) Graphic symbol

- Set(J), Reset(K), Complement(J=K=1)
- $D = JQ' + K'Q$

T flip-flop

 

- Complementing flip-flop
- $D = TQ' + T'Q$


Flip-Flop Characteristic Tables

<i>J/K</i> Flip-Flop			
<i>J</i>	<i>K</i>	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement


<i>D</i> Flip-Flop		
<i>D</i>	$Q(t + 1)$	
0	0	Reset
1	1	Set

<i>T</i> Flip-Flop		
<i>T</i>	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

D flip-flop with asynchronous reset

 

(a) Circuit diagram

 


(b) Graphic symbol

R	Clk	D	Q	Q'
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

(c) Function table

Example of sequential circuit

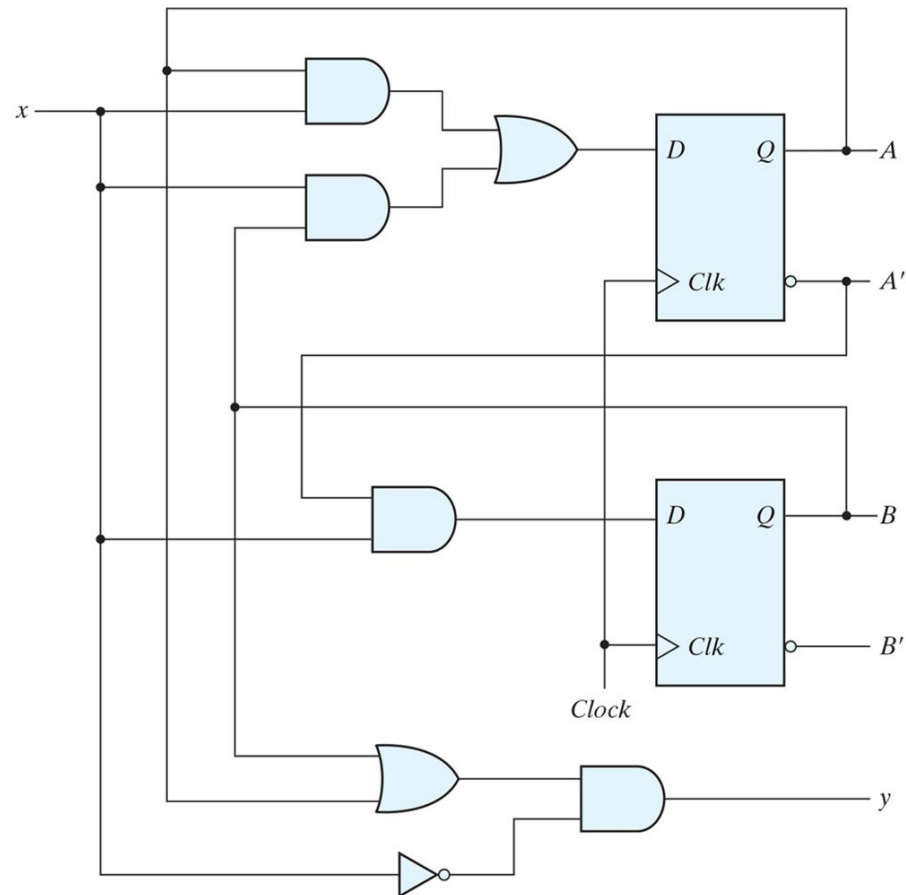

Analysis of clocked sequential circuit

- Behavior of clocked sequential circuit is determined from input, output and present state
- Outputs and next states are a function of inputs and present states

State Equations

- Specifies the next state and output as a function of the present state and inputs
- $A(t+1) = Ax + Bx$
- $B(t+1) = A'x$
- $Y = (A+B)x'$

 


Fig. 5-15 Example of Sequential Circuit

State Table for the Circuit of Fig. 5.15


Present State		Input	Next State		Output
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Second Form of the State Table


Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>y</i>	<i>y</i>
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

State diagram of the circuit of Fig. 5.15

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

 


Sequential circuit with *D* flip-flop

 

(a) Circuit diagram


Present state	Inputs		Next state
<i>A</i>	<i>x</i>	<i>y</i>	<i>A</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) State table

 

(c) State diagram

Sequential circuit with *JK* flip-flop

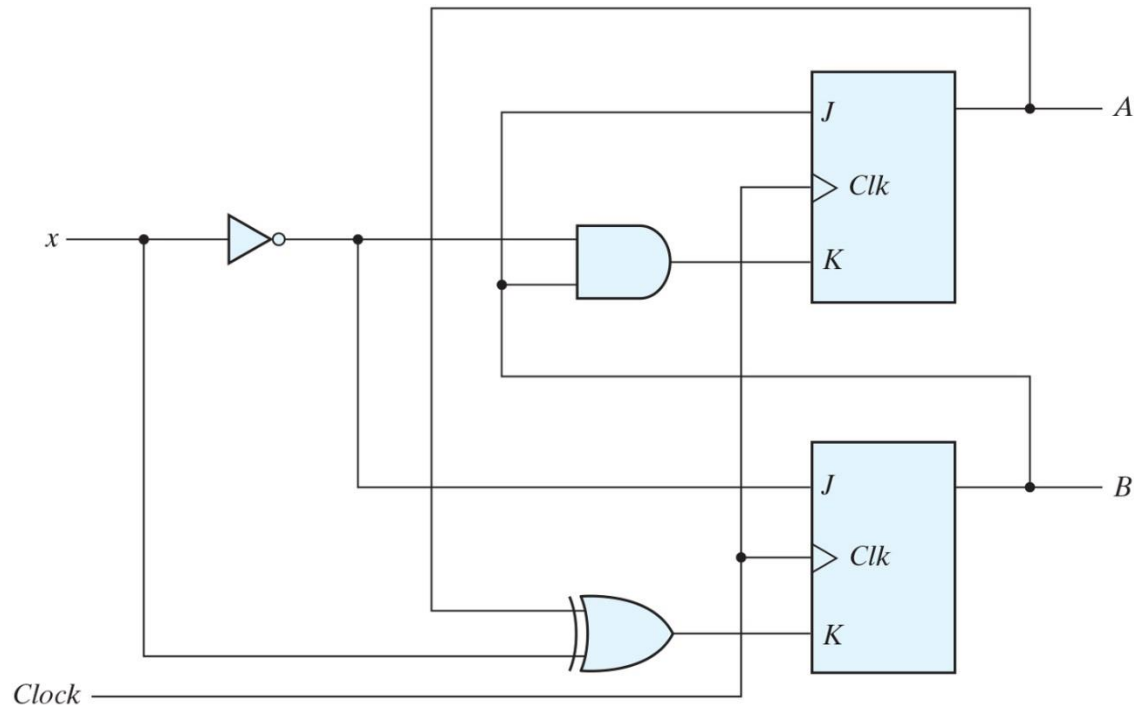


- State equation is not the same as the input equation
- Characteristic table or characteristic equation is needed
- Input equations
 - $J_A = B$ $K_A = Bx'$
 - $J_B = x'$ $K_B = A'x + Ax'$


State Table for Sequential Circuit with JK Flip-Flops

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

 State diagram of the circuit of Fig. 5.18



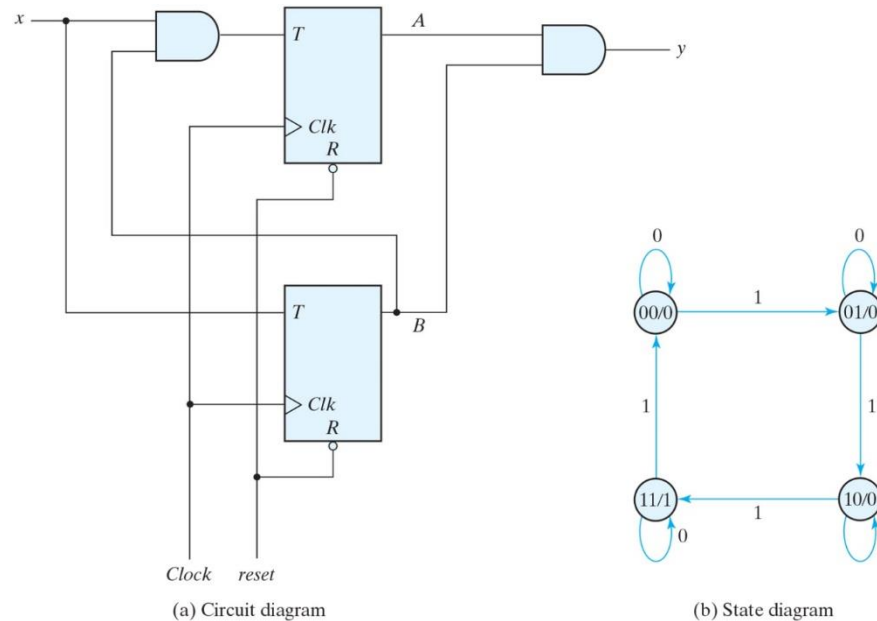Sequential circuit with T flip-flops (Binary Counter)





- Input equations and output equation
 - $T_A = Bx$, $T_B = x$
 - $y = AB$
- State equations are derived from characteristic equation
 - $A(t+1) = T_A A' + T_A A$
 - $B(t+1) = T_B B' + T_B B$

State Table for Sequential Circuit with T Flip-Flops

Present State		Input	Next State		Output
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

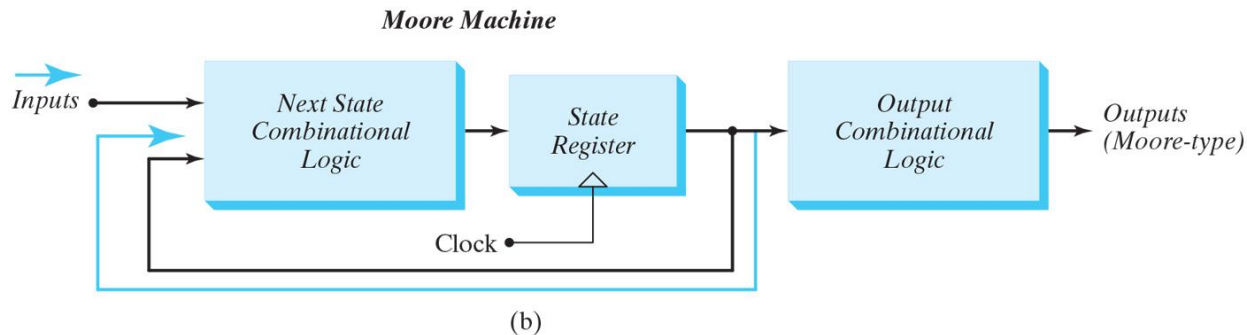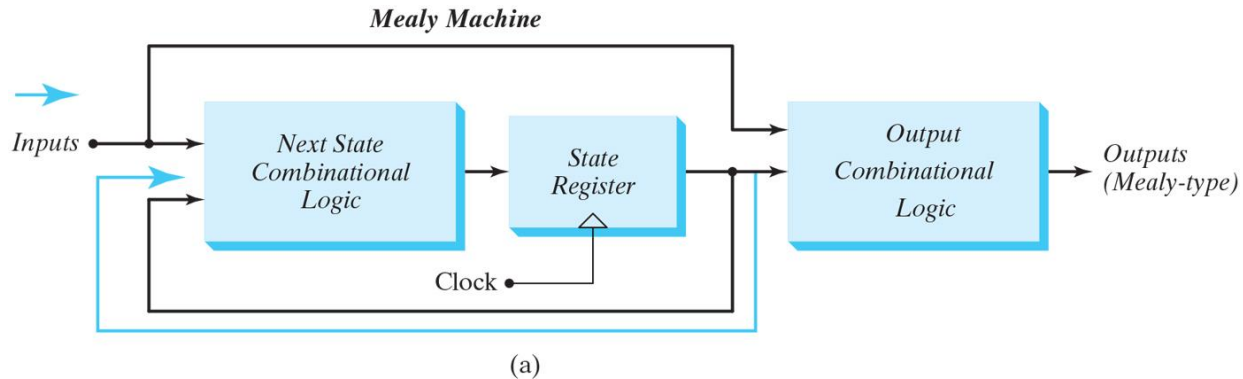Block diagrams of Mealy and Moore state machines




- Mealy model : output is a function of the present state and input
 - Inputs must be synchronized with the clock
 - Outputs must be sampled at the clock edge
- Moore model : output is a function of the present state only

State Reduction

- State reduction is used to reduce the number of flip-flop and gates
- Only input/output sequences are important
- Interested in present states that go to the same next state and have the same output

State diagram

 

State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1




Reducing the State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>e</i>	<i>f</i>	0	1



Reduced State diagram

 

Reduced the State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1

Three Possible Binary State Assignments

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000

- m states circuit, codes must contain n bits where $2^n \geq m$
- Three possible binary state assignments

Reduced State Table with Binary Assignment 1


Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
000	000	001	0	0
001	010	011	0	0
010	000	011	0	0
011	100	011	0	1
100	000	011	0	1

Design Procedure

- Sequential circuit design : requires state table
 \Leftrightarrow Combinational circuit : truth table
- The number of flip-flop is determined from the number of states
 - If 2^n states exist, there are n flip-flops
- Design steps
 - 1) Derive a state diagram or state table
 - 2) Reduce the number of states if necessary
 - 3) Assign binary code to the state
 - 4) Choose the type of flip-flops to be used
 - 5) Derive the flip-flop input equations and output equations
 - 6) Draw the logic diagram

State diagram for sequence detector

 Three or more consecutive 1's in a string of bits coming through an input line



State Table for Sequence Detector

Present State		Input	Next State		Output
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

K-Maps for sequence detector

Bx		B			
		00	01	11	10
A	0	m_0	m_1	m_3 1	m_2
	1	m_4	m_5 1	m_7 1	m_6

x

$$D_A = Ax + Bx$$

Bx		B			
		00	01	11	10
A	0	m_0	m_1 1	m_3	m_2
	1	m_4	m_5 1	m_7 1	m_6

x


$$D_B = Ax + B'x$$

Bx		B			
		00	01	11	10
A	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7 1	m_6 1

x

$$y = AB$$

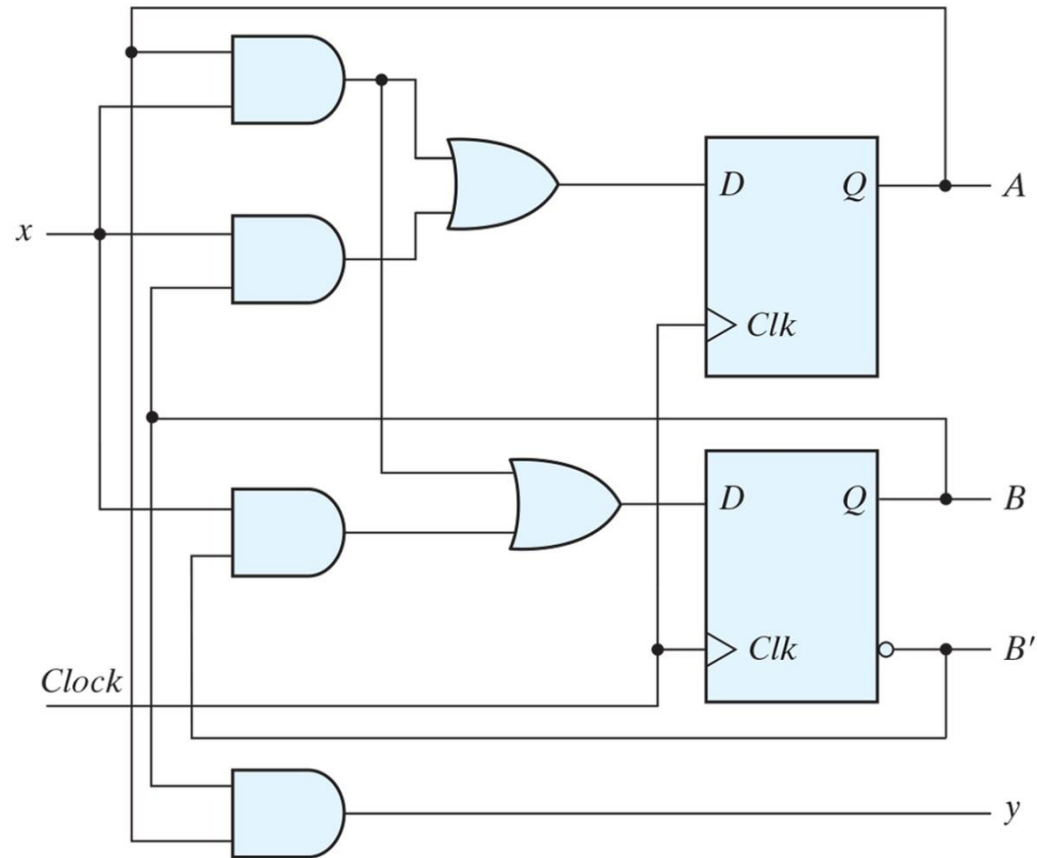Logic diagram of a Moore-type sequence detector



Flip-Flop Excitation Tables

$Q(t)$	$Q(t = 1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

(a) JK Flip-Flop

$Q(t)$	$Q(t = 1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

(b) T Flip-Flop

State Table and JK Flip-Flop Inputs

Present State		Input	Next State		Flip-Flop Inputs			
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	<i>J_A</i>	<i>K_A</i>	<i>J_B</i>	<i>K_B</i>
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

Maps for J and K input equations

		B			
		00	01	11	10
A	0	m_0	m_1	m_3	m_2 1
	1	m_4 X	m_5 X	m_7 X	m_6 X

x
 $J_A = Bx'$

		B			
		00	01	11	10
A	0	m_0 X	m_1 X	m_3 X	m_2 X
	1	m_4	m_5	m_7 1	m_6

x
 $K_A = Bx$


		B			
		00	01	11	10
A	0	m_0	m_1 1	m_3 X	m_2 X
	1	m_4	m_5 1	m_7 X	m_6 X

x
 $J_B = x$

		B			
		00	01	11	10
A	0	m_0 X	m_1 X	m_3	m_2 1
	1	m_4 X	m_5 X	m_7 1	m_6


x
 $K_B = (A \oplus x)'$

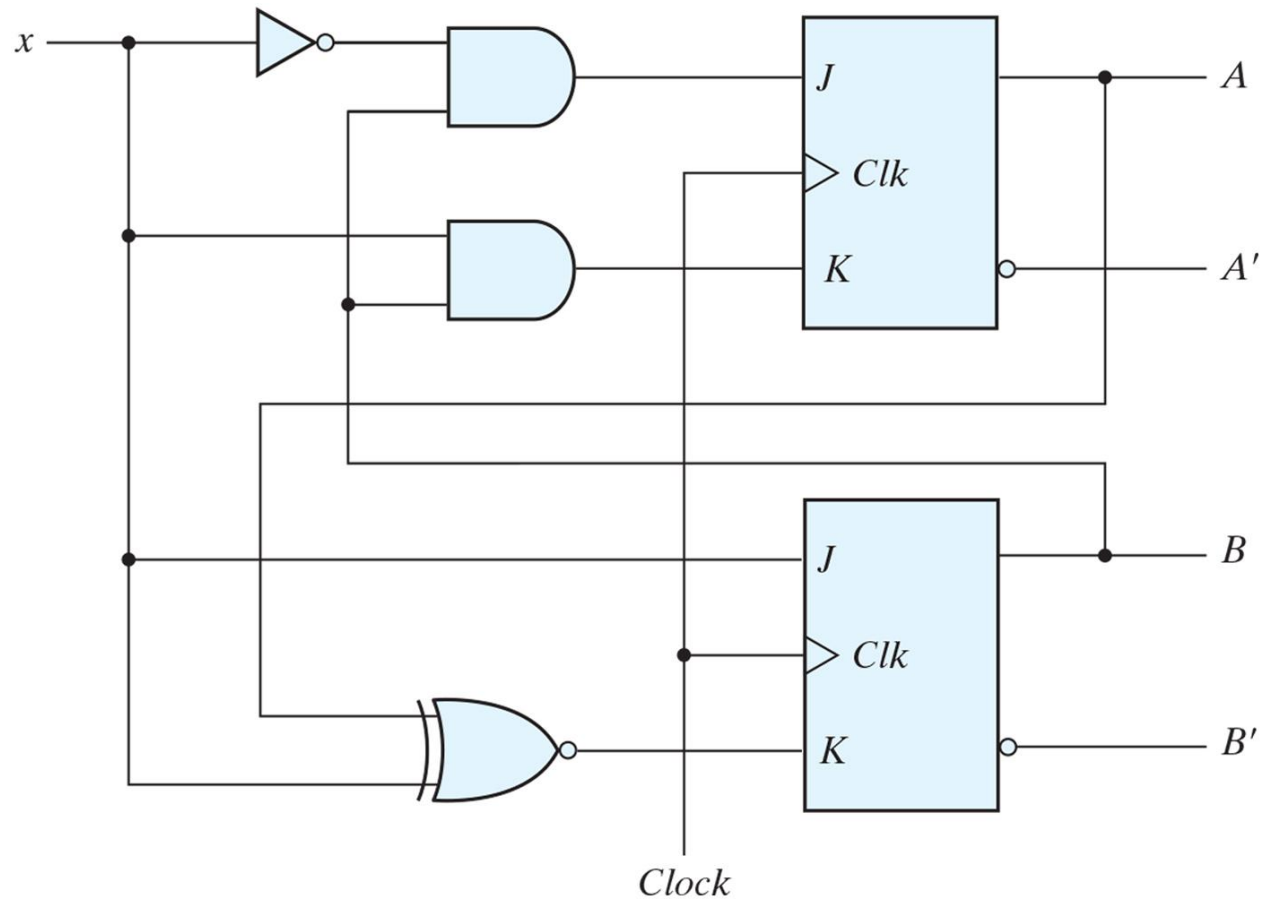Logic diagram for sequential circuit with *JK* flip-flops



State diagram of three-bit binary counter

 3-bit counter has 3 flip-flops and can count from 0 to 2^n-1 ($n=3$)



State Table for Three-Bit Counter

Present State			Next State			Flip-Flop Inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_{A2}	T_{A1}	T_{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

Maps for three-bit binary counter

$A_2 \backslash A_1 A_0$		A_1			
		00	01	11	10
A_2	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

Map 1: $T_{A_2} = A_1 A_0$. The cells m_3 and m_7 are shaded blue and contain the value 1.

$A_2 \backslash A_1 A_0$		A_1			
		00	01	11	10
A_2	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

Map 2: $T_{A_1} = A_0$. The cells m_1, m_3, m_5, m_7 are shaded blue and contain the value 1.

$A_2 \backslash A_1 A_0$		A_1			
		00	01	11	10
A_2	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

Map 3: $T_{A_0} = 1$. All cells are shaded blue and contain the value 1.

Logic diagram of three-bit binary counter

